

ganeshprabhu2005 / T-FLIPFLOP-POSEDGE

<> Code Pull requests Actions Projects Wiki Security Insights Settings

GPL-3.0 license

0 stars 86 forks 0 watching 1 Branch 0 Tags Activity

Public repository · Forked from [naavaneetha/T-FLIPFLOP-POSEDGE](#)

main 1 Branch 0 Tags Go to file Go to file Add file Code

This branch is 1 commit ahead of [naavaneetha/T-FLIPFLOP-POSEDGE:main](#) . Contribute Sync fork

ganeshprabhu2005 Update README.md now

db	EXP9	3 months ago
incremental_db	EXP9	3 months ago
output_files	EXP9	3 months ago
simulation	EXP9	3 months ago
LICENSE	Initial commit	3 months ago
README.md	Update README.md	now
TFLIPFLOPPOSEDGE.qpf	EXP9	3 months ago
TFLIPFLOPPOSEDGE.qsf	EXP9	3 months ago
TFLIPFLOPPOSEDGE.qws	EXP9	3 months ago
TFLIPFLOPPOSEDGE.v	EXP9	3 months ago
TFLIPFLOPPOSEDGE.v.bak	EXP9	3 months ago
Waveform.vwf	EXP9	3 months ago

README License

T-FLIPFLOP-POSEDGE

AIM:


To implement T flipflop using verilog and validating their functionality using their functional tables

SOFTWARE REQUIRED:

Quartus prime

THEORY**T Flip-Flop**

 T flip-flop is the simplified version of JK flip-flop. It is obtained by connecting the same input 'T' to both inputs of JK flip-flop. It operates with only positive clock transitions or negative clock transitions. The circuit diagram of T flip-flop is shown in the following figure.



This circuit has single input T and two outputs Q_t & Q_{t+1} . The operation of T flip-flop is same as that of JK flip-flop. Here, we considered the inputs of JK flip-flop as $J = T$ and $K = T$ in order to utilize the modified JK flip-flop for 2 combinations of inputs. So, we eliminated the other two combinations of J & K, for which those two values are complement to each other in T flip-flop. The following table shows the state table of T flip-flop.

Here, Q_t & Q_{t+1} are present state & next state respectively. So, T flip-flop can be used for one of these two functions such as Hold, & Complement of present state based on the input conditions, when positive transition of clock signal is applied. The following table shows the characteristic table of T flip-flop. Inputs Present State Next State

Inputs	Present State	Next State
T	Q_t	Q_{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

From the above characteristic table, we can directly write the next state equation as $Q(t+1) = T'Q(t) + TQ(t)'$
 $\Rightarrow Q(t+1) = T \oplus Q(t)$

Procedure

Step 1: Open Quartus II in your laptop.

Step 2: Write code to implement SR flipflop using verilog and validating their functionality using their functional tables.

Step 3: Run compilation to check for errors.

Step 4: Open waveform output and load input values.

Step 5: Run simulation to get the output.

Step 6: Open in RTL viewers to get RTL diagram output.


PROGRAM

/* Program for flipflops and verify its truth table in quartus using Verilog programming. Developed by: GANESH PRABHU J RegisterNumber: 212223220023


```
module TFLIPFLOPPOSEDGE( input clk, rst_n, input t,
    output reg q,
    output q_bar
);
always@(posedge clk)
begin
if(!rst_n)
q<=0;
else
if(t)
q<=~q;
else
q<=q;
end
assign q_bar = ~q;
endmodule
```



RTL LOGIC FOR FLIPFLOPS

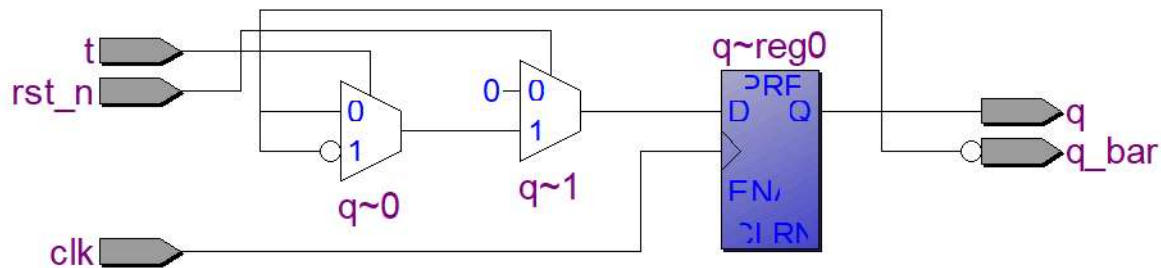

TIMING DIGRAMS FOR FLIP FLOPS

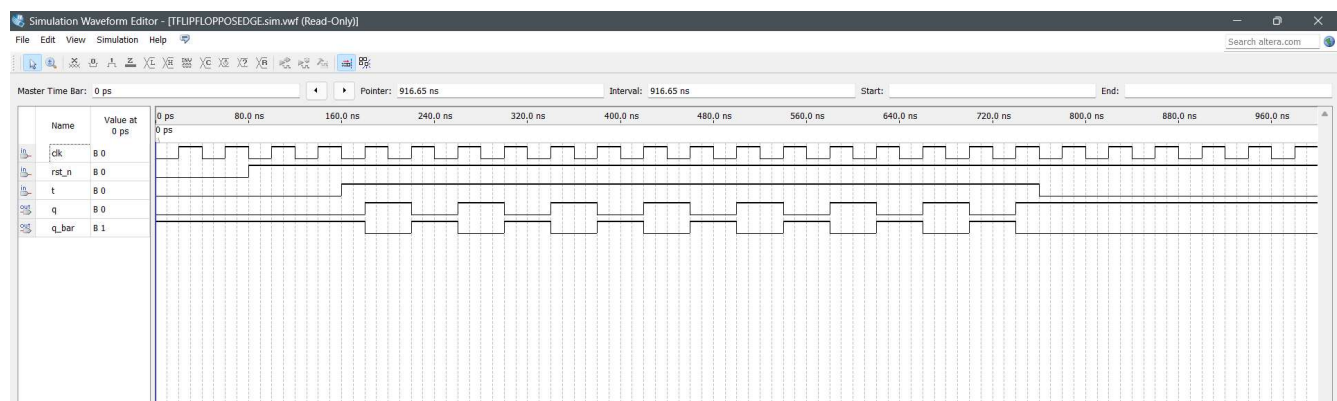

RESULTS Hence, T flipflop using verilog and validating their functionality using their functional tables is implemented.



Releases

No releases published

[Create a new release](#)

Packages

No packages published

[Publish your first package](#)

Languages

● VHDL 48.8% ● Stata 19.2% ● HTML 17.1% ● Verilog 13.4% ● Standard ML 1.5%

Suggested workflows

Based on your tech stack



SLSA Generic generator

Generate SLSA3 provenance for your existing release workflows

Configure



Jekyll using Docker image

Package a Jekyll site using the jekyll/builder Docker image.

Configure

[More workflows](#)

Dismiss suggestions